

Electrical Circuits

DC Circuit Analysis Quiz – Answer Key

1. **(C) 2Ω .** For parallel resistors: $1/R_{eq} = 1/6 + 1/6 + 1/6 = 3/6 = 1/2$, so $R_{eq} = 2\Omega$.
2. **(B) The sum of currents entering a node equals the sum leaving.** KCL is based on conservation of charge—no charge accumulates at a node: $\sum I_{in} = \sum I_{out}$.
3. **(B) 36W.** Current $I = V/R = 12/4 = 3A$. Power $P = I^2R = 9 \times 4 = 36W$. Or $P = V^2/R = 144/4 = 36W$.
4. **(B) Current.** In series, components share the same current path. Voltage divides across components; total resistance is the sum of individual resistances.
5. **(B) $R \times C$.** Time constant $\tau = RC$ (in seconds when R in ohms, C in farads). After one time constant, capacitor charges to 63.2% of final value.
6. **True.** An ideal voltage source has zero internal resistance and maintains constant terminal voltage regardless of load current (infinite current capability in theory).
7. **False.** Thevenin's theorem states a linear circuit can be replaced by a voltage source in series with a resistor (V_{Th} in series with R_{Th}). Norton's theorem uses a current source in parallel with a resistor.
8. **True.** Maximum power transfer theorem: P_{max} occurs when $R_{load} = R_{source}$. At this point, efficiency is 50% (half the power dissipated in source resistance).

9. Kirchhoff's Voltage Law (KVL):

- Statement: The algebraic sum of voltages around any closed loop equals zero
- Based on conservation of energy
- Sign convention: Voltage rises positive, drops negative (or vice versa, consistently)
- Equation: $\sum V = 0$ around any closed path

Kirchhoff's Current Law (KCL):

- Statement: Sum of currents entering a node equals sum leaving
- Based on conservation of charge
- Equation: $\sum I_{in} = \sum I_{out}$ or $\sum I = 0$ (with sign convention)

Analysis procedure:

- (a) Identify nodes and assign node voltages or loop currents
- (b) Apply KCL at each node (for nodal analysis)
- (c) Apply KVL around each independent loop (for mesh analysis)
- (d) Solve simultaneous equations

Example (two-loop circuit): Loop 1: $V_s - I_1 R_1 - (I_1 - I_2) R_2 = 0$ Loop 2: $(I_2 - I_1) R_2 - I_2 R_3 = 0$

10. Thevenin's Theorem:

- Any linear two-terminal circuit can be replaced by a voltage source V_{Th} in series with a resistance R_{Th}
- V_{Th} = open-circuit voltage across terminals
- R_{Th} = equivalent resistance seen from terminals with sources deactivated (voltage sources shorted, current sources opened)

Norton's Theorem:

- Any linear two-terminal circuit can be replaced by a current source I_N in parallel with a resistance R_N
- I_N = short-circuit current between terminals
- R_N = equivalent resistance (same as R_{Th})

Finding Thevenin equivalent:

- (a) Remove the load from the circuit
- (b) Calculate V_{Th} : voltage across open terminals
- (c) Calculate R_{Th} : deactivate sources, find equivalent resistance
- (d) Reconnect load to Thevenin equivalent

Relationship between Thevenin and Norton:

$$V_{Th} = I_N \times R_N$$

$$R_{Th} = R_N$$

$$I_N = V_{Th} / R_{Th}$$

Thevenin and Norton are source transformations—either can represent the same circuit behavior at the terminals.