

# Electrical Circuits

## DC Circuit Analysis Quiz

### Instructions:

- Answer all questions.
- For Questions 1–5, choose the best option.
- For Questions 6–8, mark True or False.
- For Questions 9–10, write detailed answers with circuit analysis.

1. Three resistors of  $6\Omega$  each are connected in parallel. What is the equivalent resistance?

- (A)  $18\Omega$
- (B)  $6\Omega$
- (C)  $2\Omega$
- (D)  $0.5\Omega$

2. Kirchhoff's Current Law (KCL) states that:

- (A) The sum of voltage drops around a closed loop is zero
- (B) The sum of currents entering a node equals the sum leaving
- (C) Power dissipated equals  $I^2R$
- (D) Voltage is proportional to current

3. A 12V battery is connected to a  $4\Omega$  resistor. What power is dissipated?

- (A) 3W
- (B) 36W
- (C) 48W
- (D) 144W

4. In a series circuit, which quantity remains the same through all components?

- (A) Voltage
- (B) Current
- (C) Resistance
- (D) Power

5. The time constant of an RC circuit is:
- (A)  $R/C$
  - (B)  $R \times C$
  - (C)  $1/(R \times C)$
  - (D)  $\sqrt{R \times C}$
6. An ideal voltage source maintains constant voltage regardless of the current drawn. (True/False)
7. Thevenin's theorem states any linear circuit can be replaced by a voltage source in parallel with a resistor. (True/False)
8. The maximum power transfer occurs when load resistance equals source resistance. (True/False)
9. Explain Kirchhoff's Voltage Law (KVL) and Kirchhoff's Current Law (KCL). Demonstrate how to apply both laws to analyze a circuit with multiple loops and nodes.
10. Describe Thevenin's theorem and Norton's theorem. Explain the process to find Thevenin equivalent circuit and demonstrate the relationship between Thevenin and Norton equivalents.